

VLSI DESIGN FLOW: RTL TO GDS

Lecture 22
Static Timing Analysis – Part I



Sneh Saurabh
Electronics and Communications
Engineering
IIT Delhi

Lecture Plan

Static Timing Analysis (STA)

- Basics of STA (this lecture)
- Subsequent Lectures:
 - Mechanics of STA
 - Advanced concepts of STA
 - Constraints



Static Timing Analysis



Basics

NPTEL

Static Timing Analysis (STA): What is done?

- Ensures that the circuit is in a valid state at each clock cycle
- Verifies that the design is capable of operating at the *given frequency*
 - Information of *frequency* comes from *constraints*
- Ensures that the design does not have *setup* or *hold* violation at flip-flop

- The analysis is based on *worst case* scenario and takes a pessimistic view wherever possible
 - Verification is done without test vector and simulation (therefore **static**)
 - Ensures that design will not have setup or hold violations for **any test vector**

| STA | Simulation |
|---|--|
| No test-vector required | Test vector required |
| No check of functionality | Checks functionality |
| Analysis performed taking pessimistic view of delays and other attributes of the design | Simulation done based on specified test vectors and delays |



Synchronous Circuit: Data Propagation

Consider a synchronous circuit shown alongside.



Assume that:

- Flip-flops are ideal
- Buffers have some delay
- Inputs at the port IN are applied as shown [using identifiers for clarity]
- State defined by the combination of values at the Q-pin
- Initial state is {PQ}

 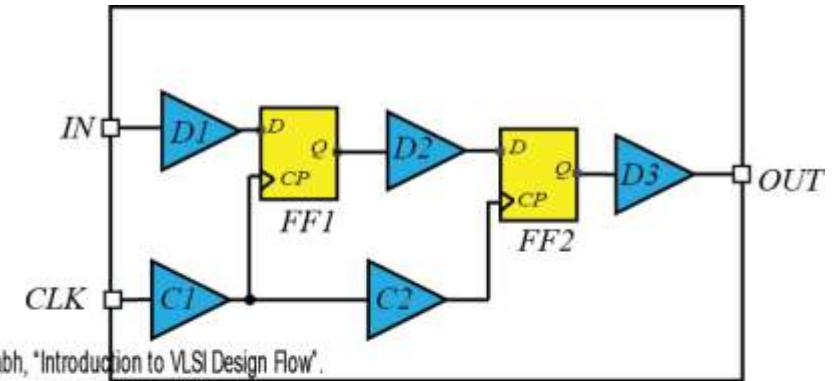Let us understand the behavior of the circuit in different clock cycles for various cases of delay of the buffers.




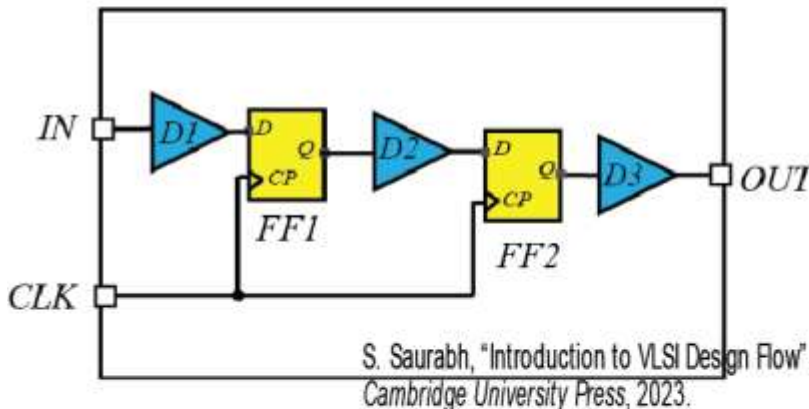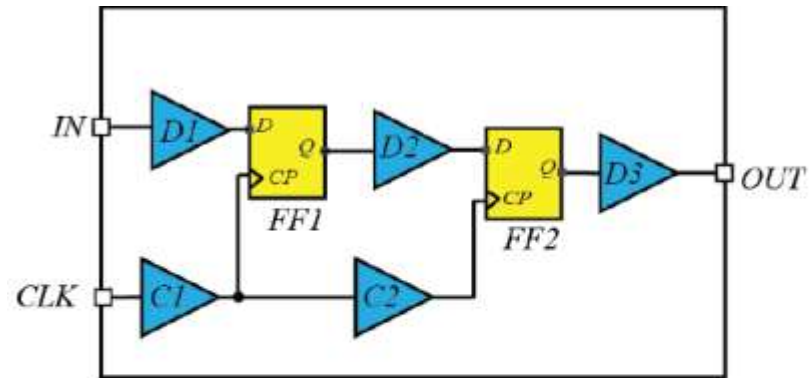Synchronous Circuit: Synchronous Behavior



Assume that:

 
- Delay of $D1$, $D2$, and $D3$ be some finite value less than the clock period, and
- Delays of $C1$ and $C2$ are negligible.



| Cycle | State |
|-------|-------|
| 1 | {PQ} |
| 2 | {AP} |
| 3 | {BA} |
| 4 | {CB} |


These are valid states of a synchronous circuit.

Synchronous Circuit: Zero Clocking

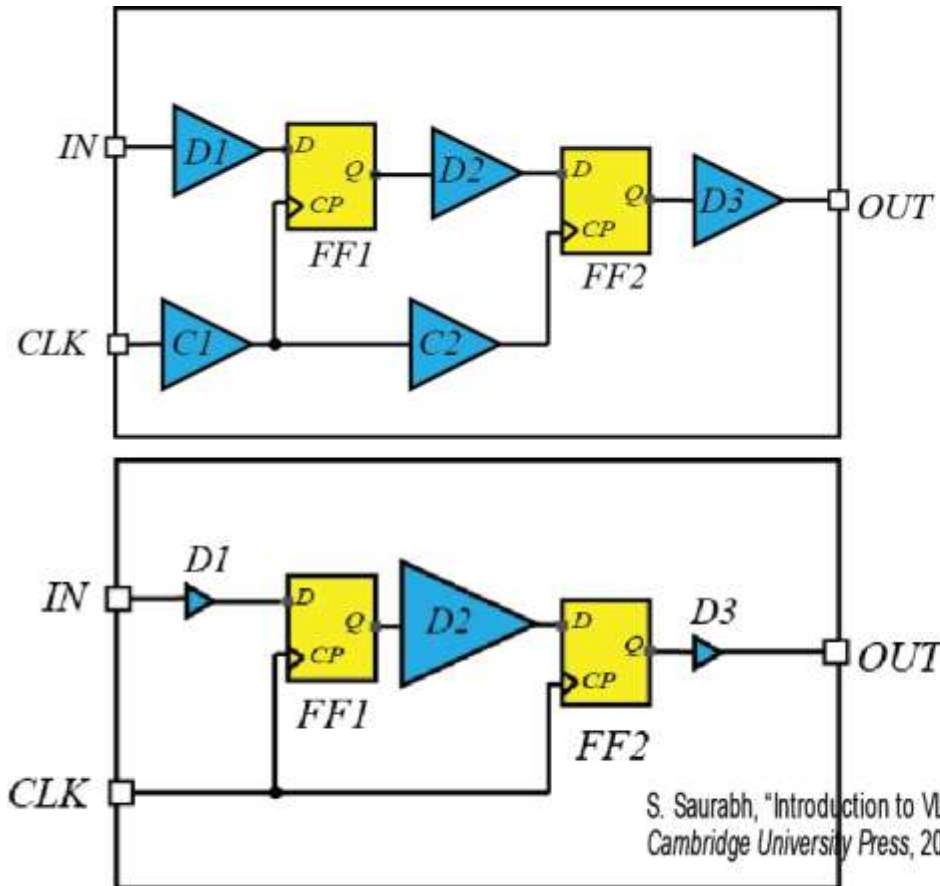

Assume that:


 
- Delay of $C1$ and $C2$ are negligible.
- Delay of the circuit element $D2$ is more than one clock period, but less than two clock periods.
- Delay of $D1$ and $D3$ are minimal.



| Cycle | State | Valid State |
|-------|-------|-------------|
| 1 | {PQ} | {PQ} |
| 2 | {AQ} | {AP} |
| 3 | {BP} | {BA} |
| 4 | {CA} | {CB} |

- In effect clock fails to capture the right data (zero-clocking) due to late data arrival
- The circuit goes into invalid states


Synchronous Circuit: Double Clocking

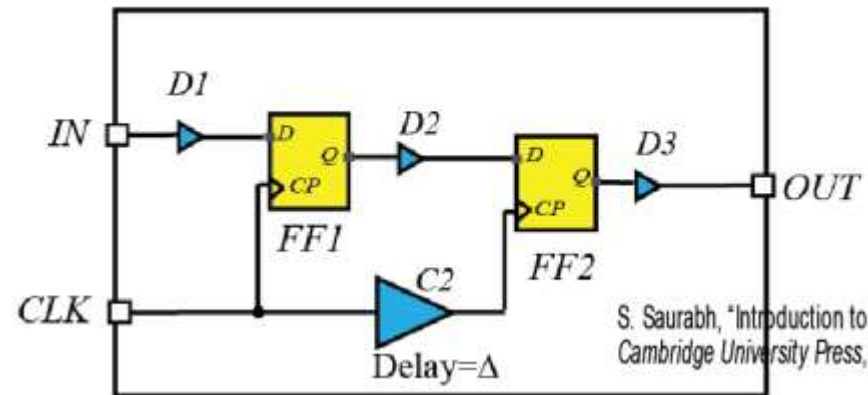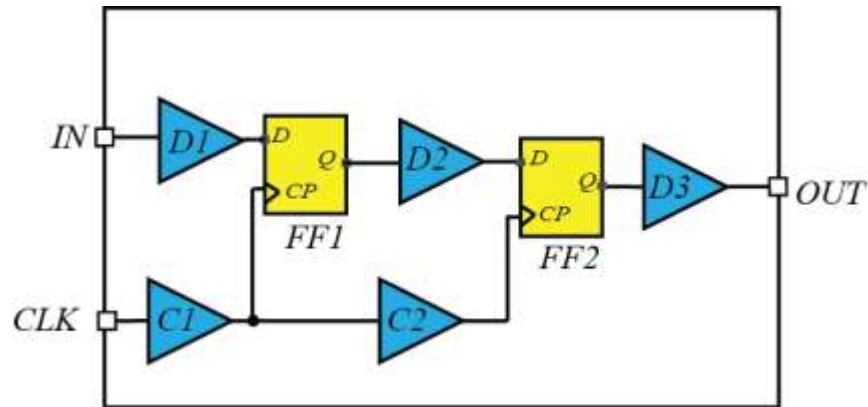

S. Saurabh, "Introduction to VLSI Design Flow",
Cambridge University Press, 2023.

Assume that:

 - Delay of circuit elements $D1$, $D2$, $D3$, and $C1$ are insignificant.
- Delay of the circuit element $C2$ is Δ




| Cycle | State | Valid State |
|-------|-------|-------------|
| 1 | {PP} | {PQ} |
| 2 | {AA} | {AP} |
| 3 | {BB} | {BA} |
| 4 | {CC} | {CB} |

- In effect, the data gets captured by two flop-flops by the same clock edge (double clocking)
- The circuit goes into invalid states

Synchronous Circuit: Verification

To ensure synchronous behavior:

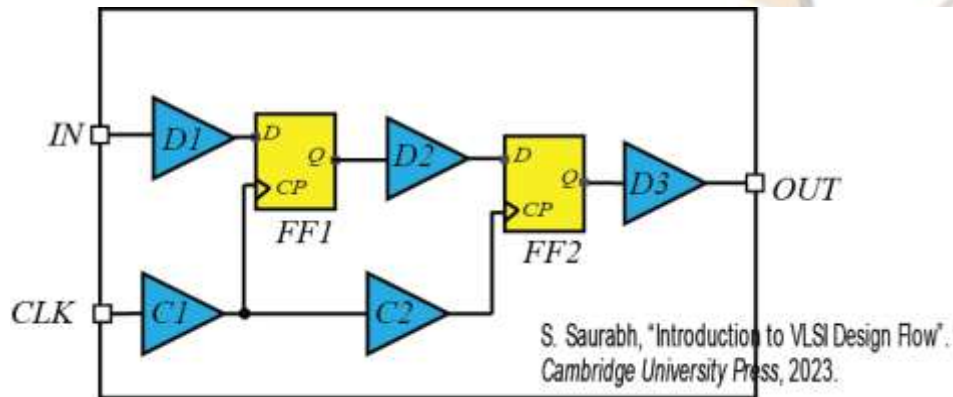
- **Avoid Zero Clocking:** setup analysis or late analysis
- **Avoid Double Clocking:** hold analysis or early analysis
- A synchronous circuit can contain many flip-flops
 - Data can propagate sequentially through a pipeline before reaching the output
- Examine each pair of launch and capture flip-flops separately



- Various types of combinational gates can be encountered in a path
- Add the delay of all the combinational circuit elements (and also the wire delay) in the path and check for delay requirements
- Real flip-flops have ST, HT, CK-Q delay
- Account for them (make the verification a bit more pessimistic)

Static Timing Analysis (STA) : Setup Requirement (1)

 - Ensures that the data sent by launch flip-flop in a given clock cycle is captured reliably by the capture flip-flop in *the next clock cycle*
- Ensures that the setup requirement of the flip-flop is also met




Arrival Time of data at the D-pin: $t_{arrival} = T_{launch} + T_{clk-ql} + T_{data}$

Required time for data to settle at FF2/D: $t_{req,set} = T_{period} + T_{capture} - T_{setup-c}$

To avoid zero clocking and setup-time constraints of flip-flops: $t_{req,set} > t_{arrival}$

Setup requirement: $T_{period} + T_{capture} - T_{setup-c} > T_{launch} + T_{clk-ql} + T_{data}$

 Static Timing Analysis (STA) : Setup Requirement (2)



Setup requirement:

$$T_{period} + T_{capture} - T_{setup-c} > T_{launch} + T_{clk-ql} + T_{data}$$

$$T_{period} > (T_{launch} - T_{capture}) + T_{clk-ql} + T_{data} + T_{setup-c}$$

$$T_{period} > \delta_{lc} + T_{clk-ql} + T_{data} + T_{setup-c} \quad [\delta_{lc} \text{ is the clock skew}]$$

Most Restrictive:

$$T_{period} > \delta_{lc} + T_{clk-ql} + T_{data,max} + T_{setup-c}$$

Setup Violations can occur if:


- Clock Period is decreased (clock frequency is increased)
- Delay of capture clock path is decreased
- Delay of data path is increased
- Delay of launch clock path is increased

What happens for an ideal flip-flop?

What happens for an ideal clocking structure?

Static Timing Analysis (STA) : Hold Requirement (1)

 - The hold check is from one active edge of the clock in the launch flip-flop to the *same clock edge* at the capture flip-flop (independent of clock-period)
- Ensures that the hold requirement of the flip-flop is also met




Data Reaches D-pin: $t_{arrival} = T_{launch} + T_{clk-ql} + T_{data}$

Data to arrive at FF2/D after the required time: $t_{req,hold} = T_{capture} + T_{hold-c}$

To avoid double clocking and hold-time constraints of flip-flops: $t_{arrival} > t_{req,hold}$

Hold requirement: $T_{launch} + T_{clk-ql} + T_{data} > T_{capture} + T_{hold-c}$

 Static Timing Analysis (STA) : Hold Requirement (2)



Hold requirement:

$$T_{launch} + T_{clk-ql} + T_{data} > T_{capture} + T_{hold-c}$$
$$\delta_{lc} + T_{clk-ql} + T_{data} > T_{hold-c}$$

Most Restrictive requirement:

$$\delta_{lc} + T_{clk-ql} + T_{data,min} > T_{hold-c}$$

- Hold Violations can occur if:
 - Delay of data path is decreased
 - Delay of launch clock path is decreased
 - Delay of capture clock path is increased

What happens for an ideal flip-flop?

What happens for an ideal clocking structure?

References

- S. Saurabh, “Introduction to VLSI Design Flow”. Cambridge: *Cambridge University Press*, 2023.

