


# VLSI DESIGN FLOW: RTL TO GDS

Lecture 15  
Logic Optimization: Part II



Sneh Saurabh  
Electronics and Communications  
Engineering  
IIT Delhi

# Lecture Plan

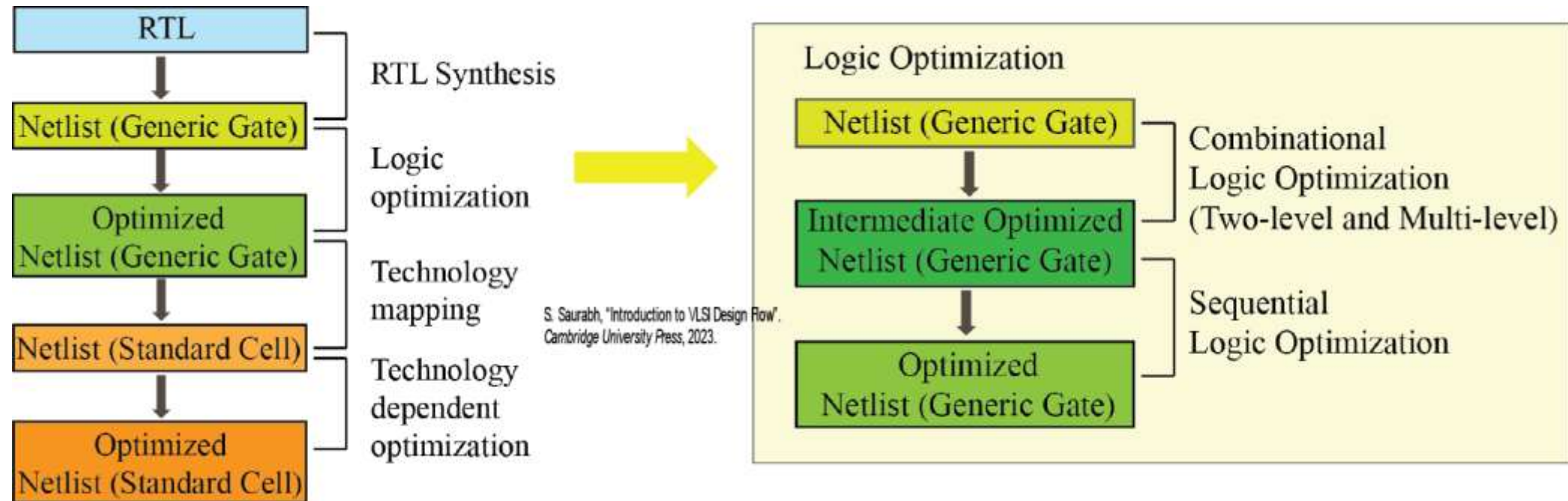

- Multilevel Logic Optimization

---

---

The NPTEL logo is centered in the background. It features a circular emblem with a stylized flower or star shape in the center, composed of multiple overlapping loops in shades of pink, orange, and yellow. Below the emblem, the word "NPTEL" is written in a bold, orange, sans-serif font.

# Multilevel Logic Optimization

# Multilevel Logic Optimization: Introduction

**Multilevel Logic:** more than two levels of logic


- Can appear naturally in RTL

## Limitations of two-level logic


- Sum of Product (SOP) representations of some functions can become too big
  - Example: parity functions, adders, and multipliers.
- Cannot reduce area by trading off speed
  - Multilevel logic circuits offer more flexibility in exploring area-delay trade-off

## Multilevel Logic Representations

- Factored Form
- Boolean Logic Network

 

 S. Saurabh, "Introduction to VLSI Design Flow".  
Cambridge University Press, 2023.



# Factored Form

A factored form consists of:

- a) literals
- b) sum (logical OR) of factored form
- c) product (logical AND) of factored form.

A factored form is an SOP, of SOP, of SOP, ..., of arbitrary depth.

- Given an SOP, it can be converted to a factored form by *factoring*
- Factoring can convert a two-level representation to a multilevel representation.

- Given an SOP, its factored form is not unique

- Consider the following Boolean function in the SOP form:  $ac + ad + bc + bd + ce$
- We can obtain a factored form representation as:

$$(a + b)(c + d) + ce$$

$$(a + b)d + (a + b + e)c$$

- Number of literals in the factored form correlates with the circuit area

# Boolean Logic Network (1)


- Boolean logic network is a directed acyclic graph
  - annotate each vertex with a single-output local Boolean function
- It can conveniently represent multilevel logic circuit with more than one output.

- Consider the following set of equations:

$$\begin{aligned}p &= a + b \\q &= ef \\r &= p + c'd + q \\s &= d' + q' \\x &= r \\y &= s\end{aligned}$$

- Assume that inputs are  $a, b, c, d, e$ , and  $f$ .
- Assume that  $x$  and  $y$  are outputs

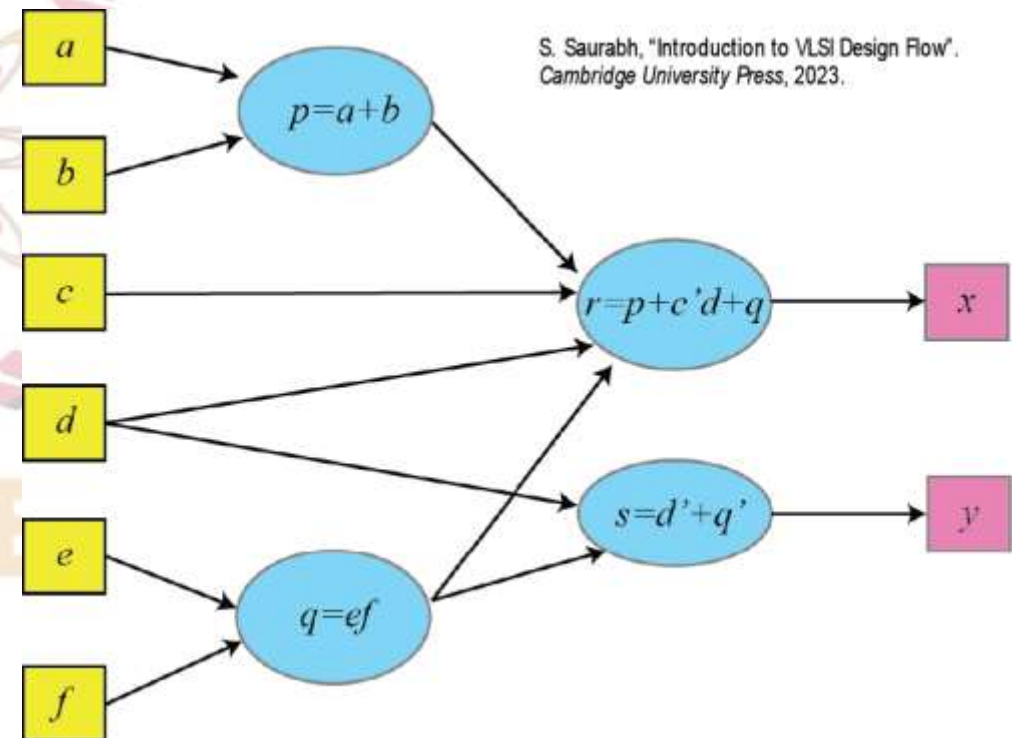- The incoming edges to a vertex denote the variables on which the local function at that vertex depends





# Boolean Logic Network (2)

---

## Flexibility of Boolean logic network:

- Local functions in a Boolean logic network can be arbitrarily complicated
- Both its underlying graph and the local functions can be manipulated during optimization
- Optimization can explore both the behavioral and the structural features of the implementation

## Estimating Area and Delay:

- Local functions restricted to be in an SOP form and made *minimal with respect to single-implicant containment*
- **Estimating area:** sum of all the literal counts of the local functions
- **Estimating delay:** number of stages of vertices in the logic network

---

---

# Multilevel Logic Optimization



Transformations




# Transformations

- Multilevel logic optimization is performed by applying transformations.
  - These transformations can be viewed as **operators** for the Boolean logic network.
- These operators applied iteratively until no more improvement in some QoR measures is possible.
  - The final QoR depends on the order of operation and is hard to predict.


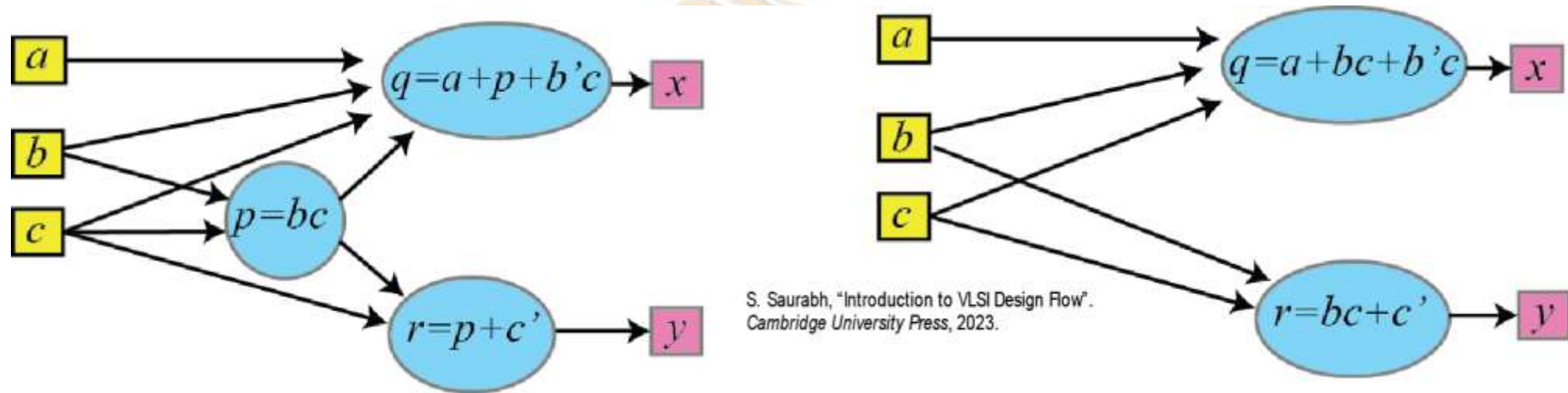
# Eliminate


- It removes a vertex from the graph and replaces all its occurrences in the network with the corresponding local function



- We carry out eliminate in the hope that subsequent transformations can reduce the cost (area)
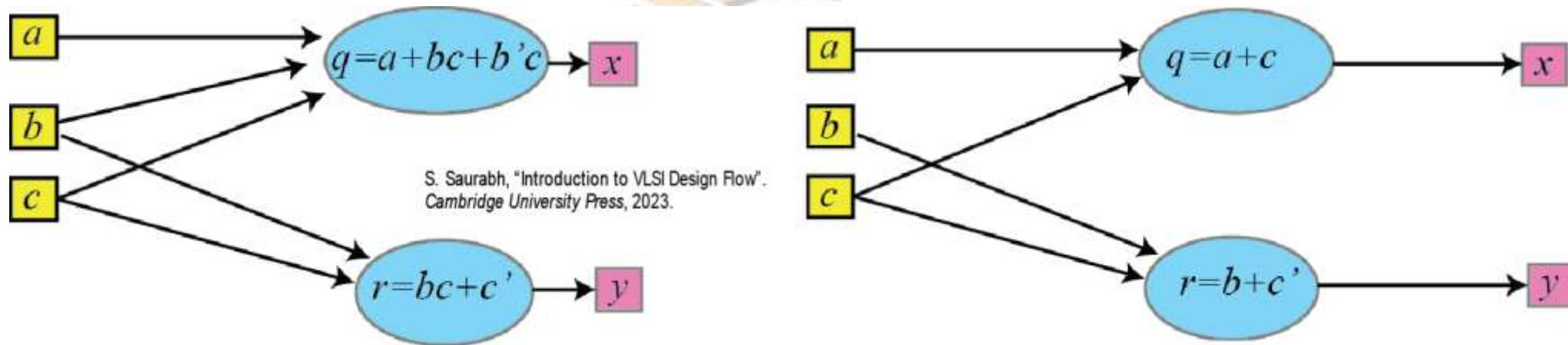
# Simplify

- It simplifies the associated local SOP expression to reduce the literal count (two-level logic optimization carried out on each local function individually)



- Reduces the literal count from 8 to 4

# Substitute


- It replaces the local function with a simpler SOP by creating new dependencies and possibly removing other dependencies.
- Creates dependencies by searching for an appropriate match.
  - It adds more structural information to the network.



- Reduces the literal count from 7 to 5
- Substitute operator needs to find whether local function  $f_i$  divides another local function  $f_j$ 
  - If it divides, we can replace  $f_j = Q \cdot f_i + R$
  - Need to perform division efficiently
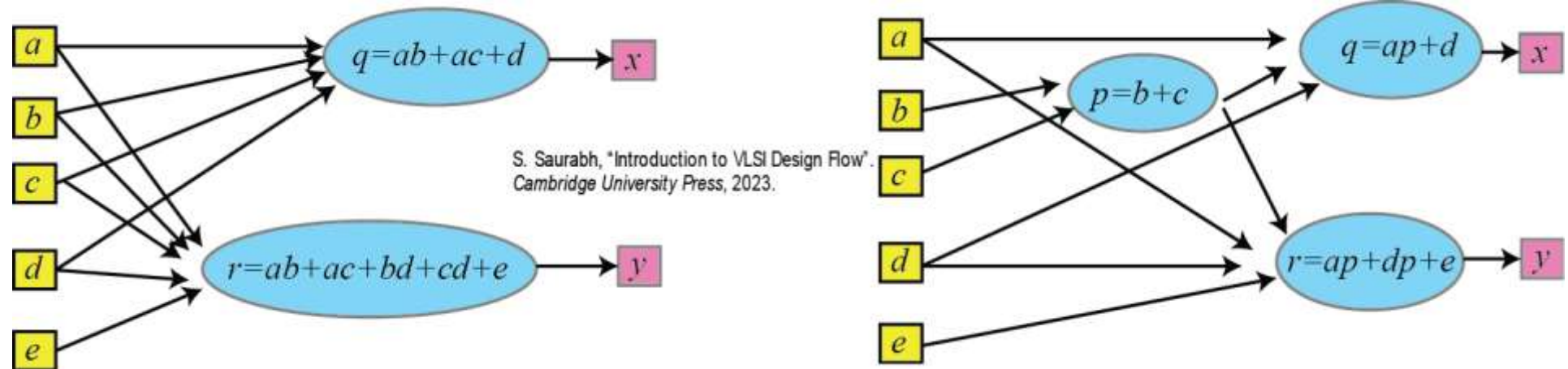
# Extract

- It finds a common subexpression for functions associated with two or more vertices.
  - Subsequently, it creates a new vertex associated with the subexpression.
  - Then replaces the common subexpressions in the original functions with the variable of the new vertex.



- Reduces the literal count from 14 to 10
- Extract operator needs to find divisors for the local functions and then search vertices with matching divisors.
  - Implementing extract operator is computationally challenging

# Challenges of Multilevel Logic Optimization

---

- Huge search space for optimization

## Division Operation:

- During multilevel logic optimization, we need to carry out division too many times.
- Practical circuits have thousands of vertices in the Boolean logic network.
  - Might need to divide each vertex with the rest [ $O(n^2)$  times, where  $n$  is the number of vertices in the Boolean logic network]
- Efficiency of division of expressions is critical for multilevel logic optimization

## Divisors:

- Need to find good divisors (one that can reduce cost) for Boolean expressions
- Finding a good set of divisors for a given Boolean expression is nontrivial

# Algebraic Model

## Algebraic Model:

- Neglecting some Boolean properties of the local functions
- Simplified model treats the local Boolean functions as polynomials and employs rules of polynomial algebra
  - Treat a variable and its complement as separate variables.

## Applications of algebraic model:

- Efficient algorithms can be designed to carry out division in the algebraic model (rather than in the Boolean model)
- Good divisors or common subexpressions in a complex Boolean logic network can be determined efficiently in a complex Boolean logic network
  - By intelligently pruning the search space (applying properties of algebraic models)



# Algebraic Model versus Boolean Model

- Algebraic model (and associated mathematics) form the basis of fast multilevel optimization in the contemporary logic optimization tools.

## Boolean Model:

- An algebraic model is weaker than a Boolean model for optimization
  - Cannot fully optimize a Boolean logic network.
- Post algebraic model-based optimization, transformations that utilize the power of the Boolean model is applied

NPTEL

---

---

# Multilevel Logic Optimization



Boolean Model

# Don't Care (DC) Conditions

---


- Don't Care (DC) conditions arise naturally in Boolean logic network
  - Due to the graph structure and dependencies among local functions.
- DCs are a rich source of optimization in multilevel logic synthesis
  - Simplifying local functions and improving the circuit's overall QoR.
- A logic synthesis tool needs to discover them using Boolean algebra (in contrast to given DCs)

There are two types of DC that are useful in simplifying local functions in a Boolean logic network:


1. Controllability Don't Cares (CDCs)
2. Observability Don't Cares (ODCs).
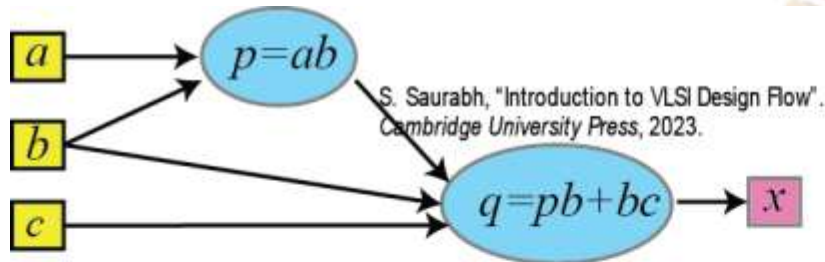
# Controllability Don't Cares (CDCs)


- The combination of input variables that can never occur at a given vertex in a Boolean logic network produces CDCs.
- Local functions can be simplified by accounting for CDCs and two-level logic minimizers



 - At the input of vertex  $q$ ,  $p = 1$  and  $b = 0$  can never occur
- $pb'$  can be treated as CDC




Cover is:  
 $q = pb + bc$

 

- Cover is:  $q = p + bc$
- Reduces the literal count by 1
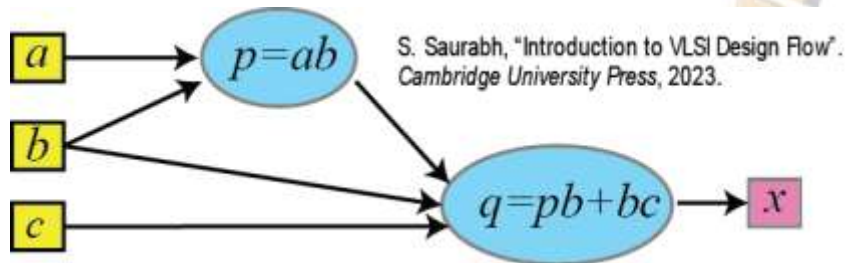
# Satisfiability Don't Cares (SDCs)

- CDCs can be computed using efficient algorithms by exploiting Satisfiability Don't Cares (SDCs).
- SDCs get enforced by the local functions associated with a vertex at its output.



Consider the vertex  $p = ab$

- The following function will never evaluate to 1:  
$$p \oplus ab = pa' + pb' + p'ab$$
- Hence, the combination of values that make the above function 1 can never occur in the network:


$$\begin{aligned} p = 1, a = 0, \\ p = 1, b = 0, \\ p = 0, a = 1, b = 1 \end{aligned}$$

- These values can be treated as DCs for the Boolean logic network

- Logic synthesis tools typically derive CDCs algorithmically using SDCs.
- Subsequently, the CDCs get utilized in simplifying local functions.

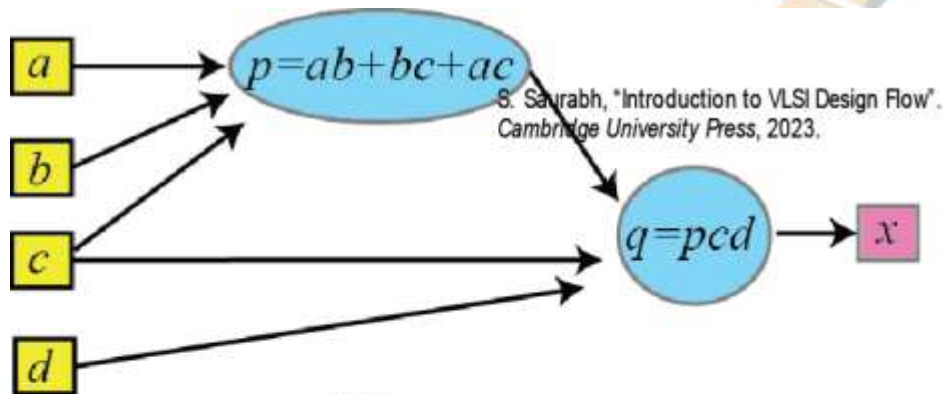
# Observability Don't Cares (ODCs)

- The ODCs are input variable combinations that obstruct the vertex output from being observed at the network output.
- We derive ODCs induced by vertices in the fanout of a given vertex.




S. Saurabh, "Introduction to VLSI Design Flow".  
Cambridge University Press, 2023.

 - If  $c = 0$ , then  $x = 0$  irrespective of  $p$
- $c = 0$ , can be treated as ODC for  $p$



Cover is:  
 $p = ab + bc + ac$

 

- Cover is:  $p = a + b$
- Literal count reduces from 9 to 5

# References

---

- G. D. Micheli. “Synthesis and Optimization of Digital Circuits”. *McGraw-Hill Higher Education*, 1994.
- S. Saurabh, “Introduction to VLSI Design Flow”. Cambridge: *Cambridge University Press*, 2023.

