


VLSI DESIGN FLOW: RTL TO GDS

Lecture 20
Formal Verification- IV



Sneh Saurabh
Electronics and Communications
Engineering
IIT Delhi

Lecture Plan

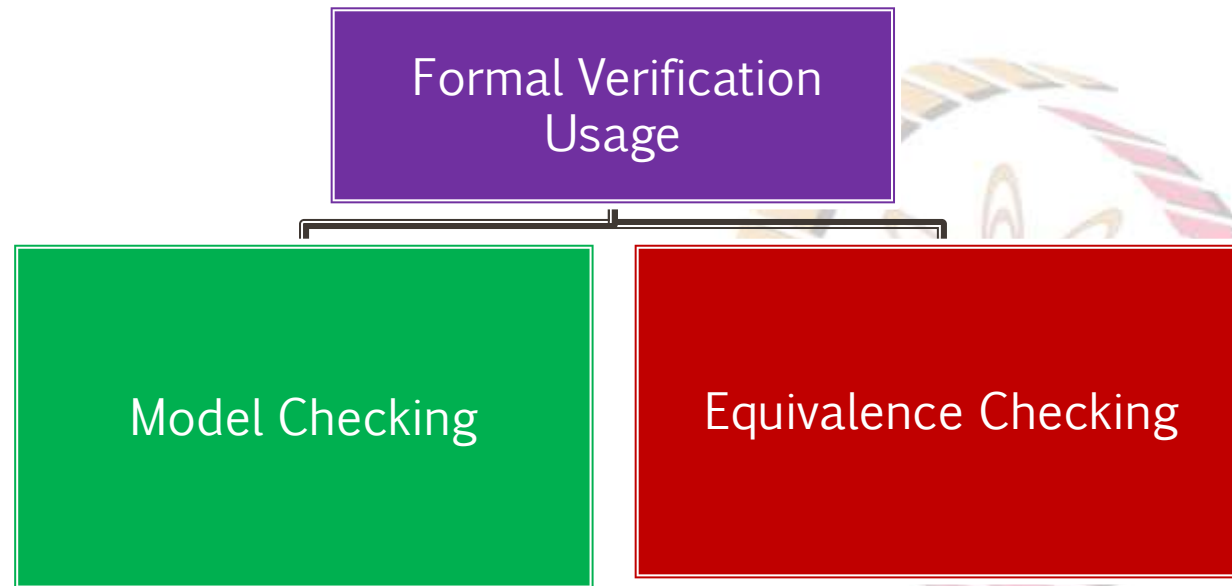


- Equivalence Checking




Formal Verification

Equivalence
Checking

Equivalence Checking: Usage

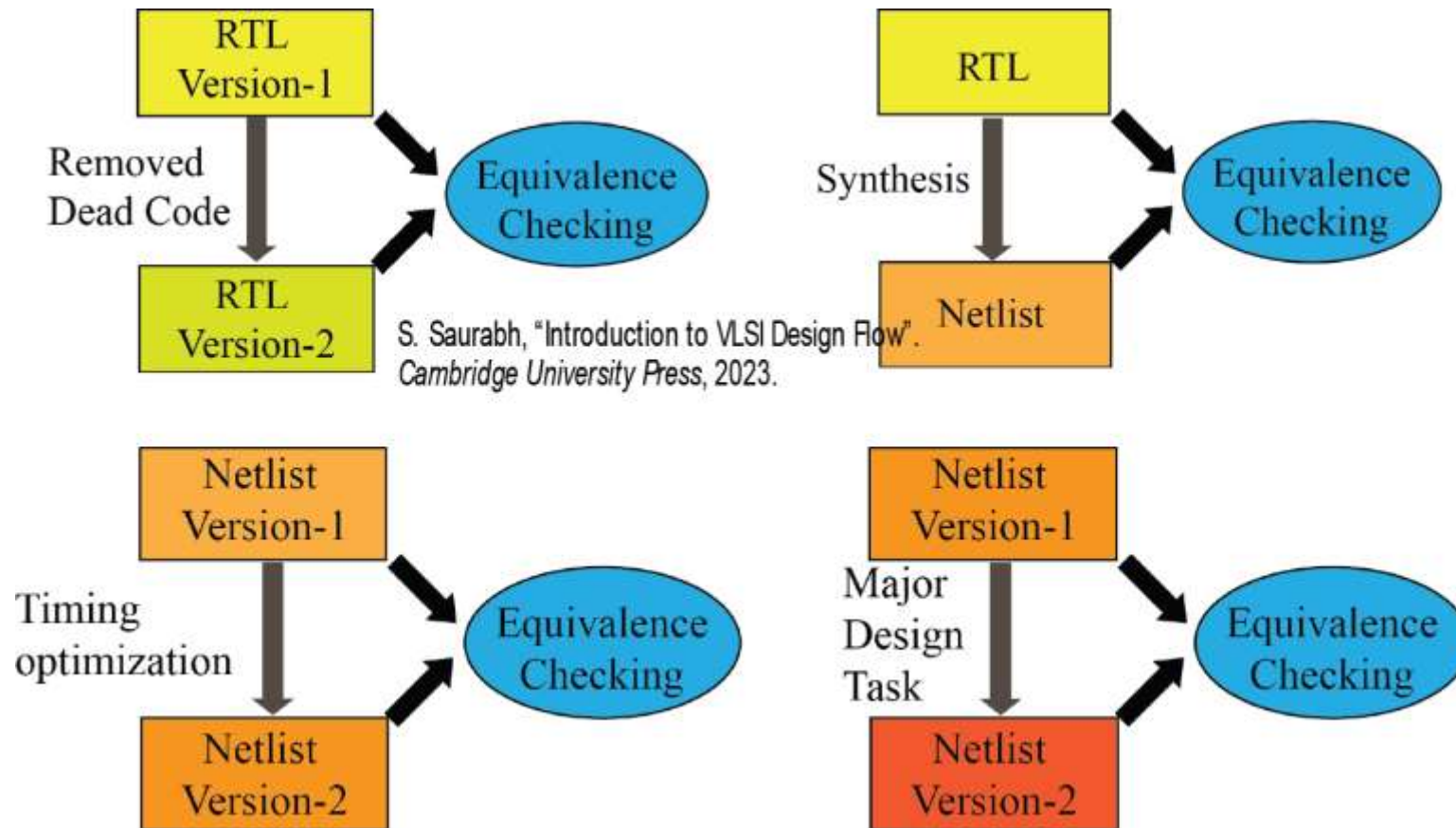

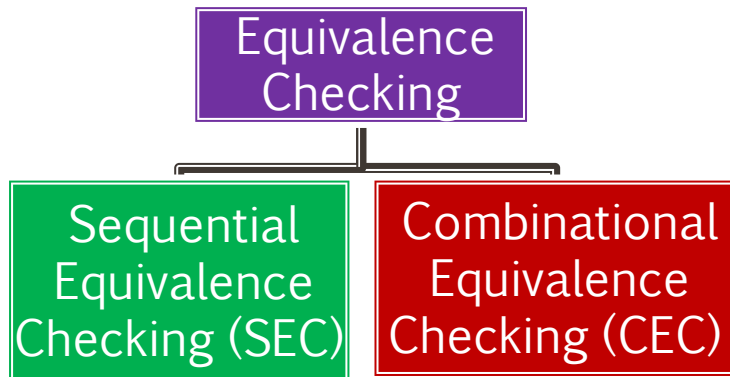Formal Verification : Equivalence Checking (2)



Sequential Equivalence Checking

- Generalized approach to comparing two models
- First convert models to FSM
- Given their initial states, it is checked whether the two FSMs produce matching output sequences for all input sequences

Challenges of SEC:

- Need to explore all reachable states
 - Encounters state explosion problem
 - Computationally difficult

Combinational Equivalence Checking


- Assume that there is a one-to-one correspondence among memory elements or flip-flops and the ports of the two models.
- Problem reduced to establishing the equivalence of pairs of combinational circuits
- Assumption holds in most cases
 - Integral part of design flows



Formal Verification


Combinational
Equivalence
Checking (CEC)

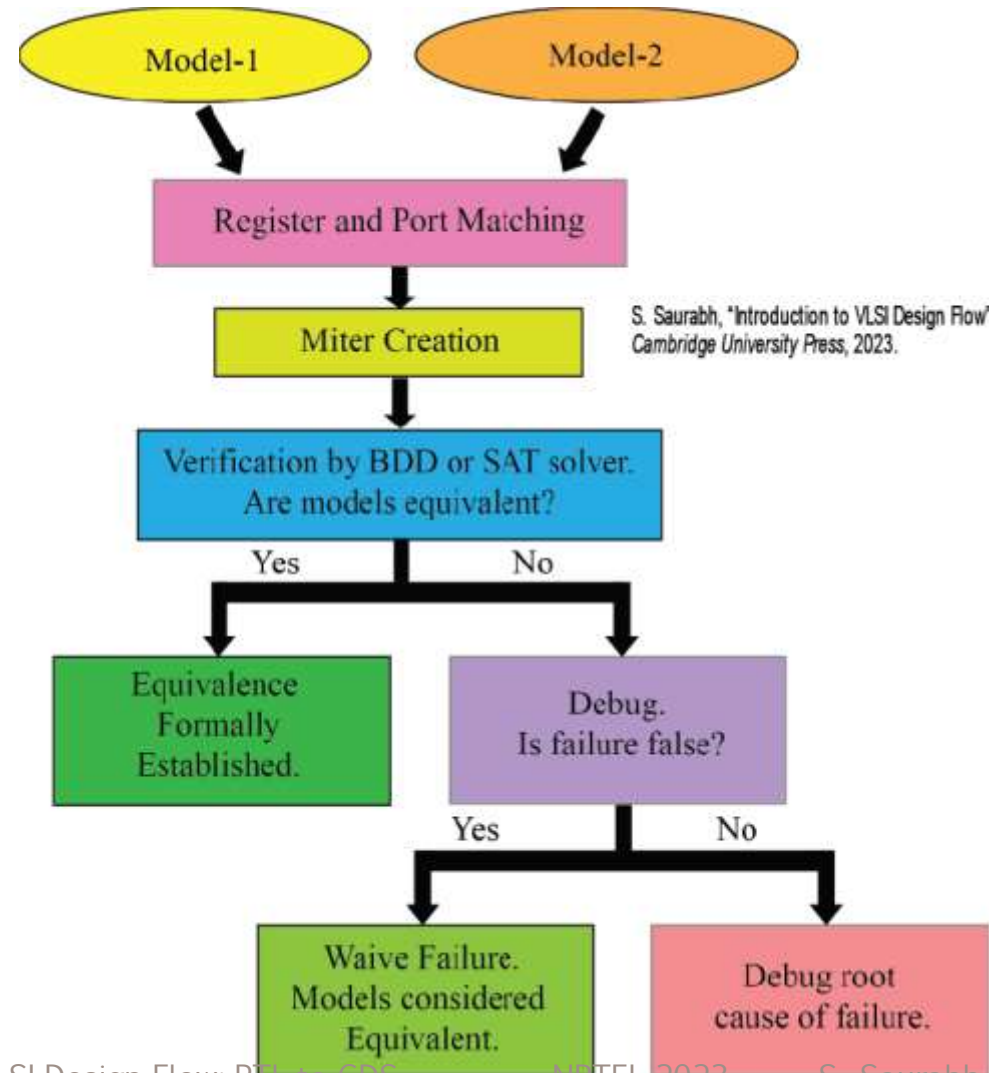Combinational Equivalence Checking (CEC): Steps




S. Saurabh, "Introduction to VLSI Design Flow".
Cambridge University Press, 2023.

 CEC: Register and Port Matching (Illustration)



Model-1

 

Model-2

CEC: Register and Port Matching (Techniques)

No exact algorithm : heuristics employed

Name-based matching:

- Works very well for I/O Ports
- Works good where a model has not undergone sequential optimization and register correspondence is kept intact
- RTL synthesis keeps names of registers based on some rules/conventions (such as add suffix to the name of signal in the RTL code)


- Sophisticated structural or functional analysis can also be used
- User can guide the tools to match the registers

```
module flip_flop_d(d, clk, q);  
    input d, clk;  
    output q;  
    reg q;  
  
    always @(posedge clk) q <= d;  
endmodule
```


S. Saurabh, "Introduction to VLSI Design Flow". *Cambridge University Press*, 2023.

CEC: Miter Creation


 
- Need to ensure that the corresponding combinational circuits lying between matched registers/ports are equivalent
- Derive multiple small combinational circuits (known as miters) from the given two models
 - A separate miter is derived for each register and output port of the two models



CEC: Miter and Equivalence

 


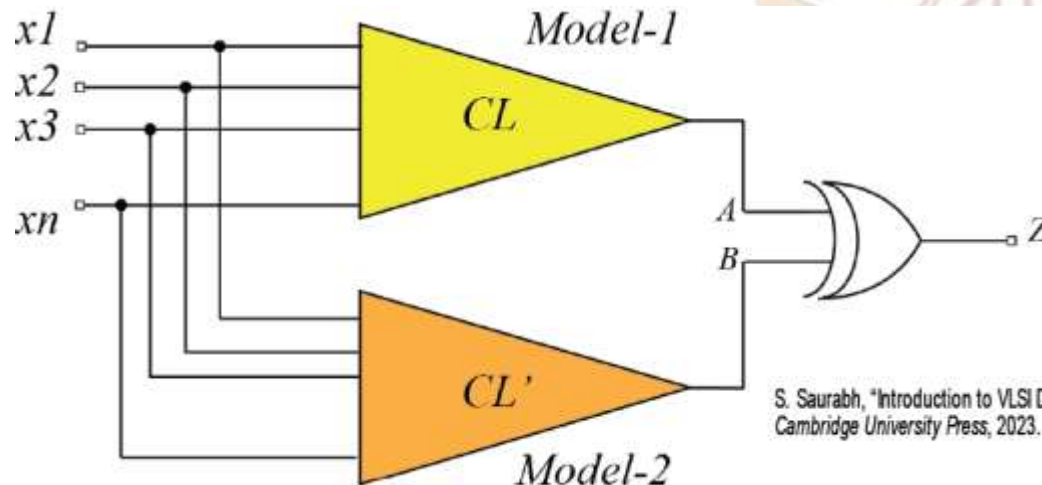
 
S. Saurabh, "Introduction to VLSI Design Flow".
Cambridge University Press, 2023.



S. Saurabh, "Introduction to VLSI Design Flow".
Cambridge University Press, 2023.

- $Z=1$ for any combination of $\{x1, x2, x3, \dots, xn\} \Rightarrow$ Model-1 and Model-2 are not equivalent
- $Z=0$ for all possible combinations of $\{x1, x2, x3, \dots, xn\} \Rightarrow$ Model-1 and Model-2 are equivalent

CEC: Illustration

   

Given two models with ports matched by names.

- Let us draw the miter circuit for checking equivalence of Model-1 and Model-2.
- Let us determine patterns of values that can be assigned to ports A and B such that the output of the miter is 1.

- A=0, B=1
- A=1, B=0

CEC: Establishing Equivalence

Using BDDs:

- Build a BDD for a miter,
 - Equivalent models: reduce to a terminal vertex with the value of 0
 - Nonequivalent models: yield some other vertex.

Using SAT Solver:

- Invoke a SAT solver on the Boolean expression representing a miter
 - Equivalent models: UNSAT
 - Nonequivalent models: SAT

CEC:

- Create miter circuits for all flip-flops and output ports in the models
- For equivalent models, all miter circuits should be equivalent

Safety and False Failures:

- CEC can sometimes give false failures
- Still it is always safe

References

- S. Saurabh, “Introduction to VLSI Design Flow”. Cambridge: *Cambridge University Press*, 2023.

