


VLSI DESIGN FLOW: RTL TO GDS

Lecture 12
RTL Synthesis- Part I



Sneh Saurabh
Electronics and Communications
Engineering
IIT Delhi

Lecture Plan

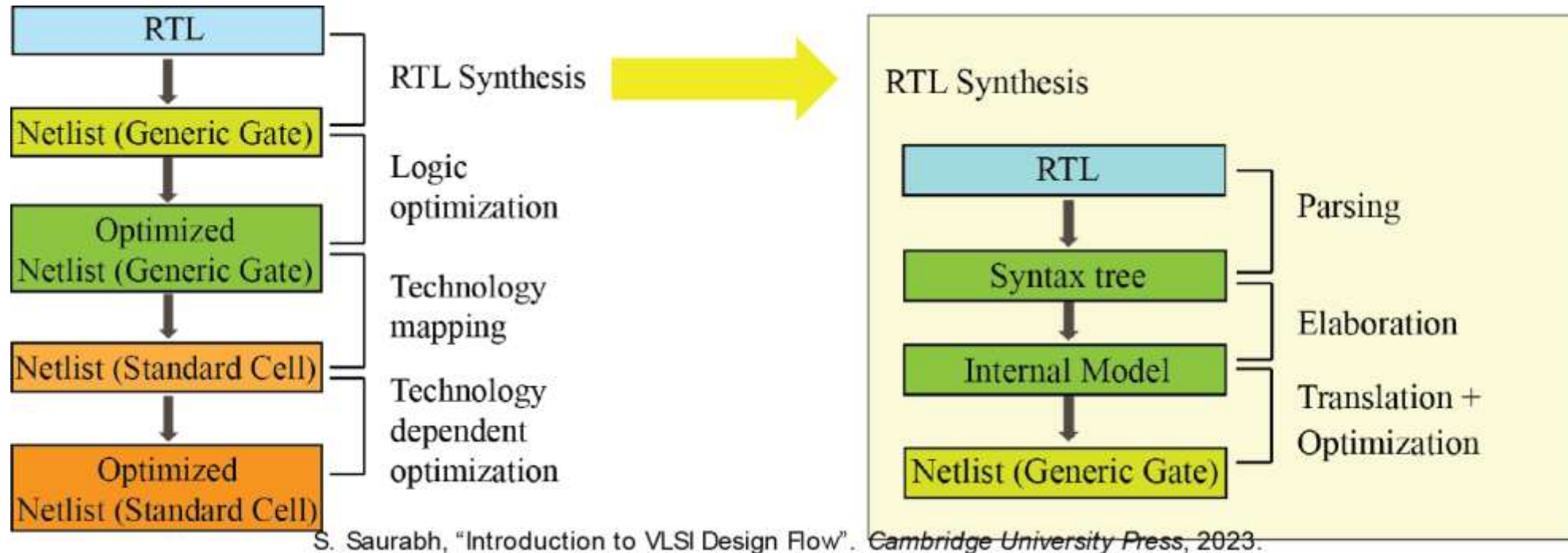

RTL synthesis:

- Initial part of logic synthesis that translates the Verilog code into netlist of generic logic gates

- Parsing, Elaboration
- Translation of some Verilog Constructs to Circuit

RTL Synthesis



Tasks


RTL Synthesis: Parsing

- Reads the given RTL files and populates a data structure for further processing

- Lexical analysis: keywords, identifiers
- Grammar/syntax checking
- Syntax tree built:
 - If grammar is correct
 - Hierarchical data structure

```
module top ();  
endmodule  
  
module mid ();  
...  
  always @ (*)  
  begin  
    a <= x+y;  
    b <= 0;  
    c = x;  
  end  
endmodule
```

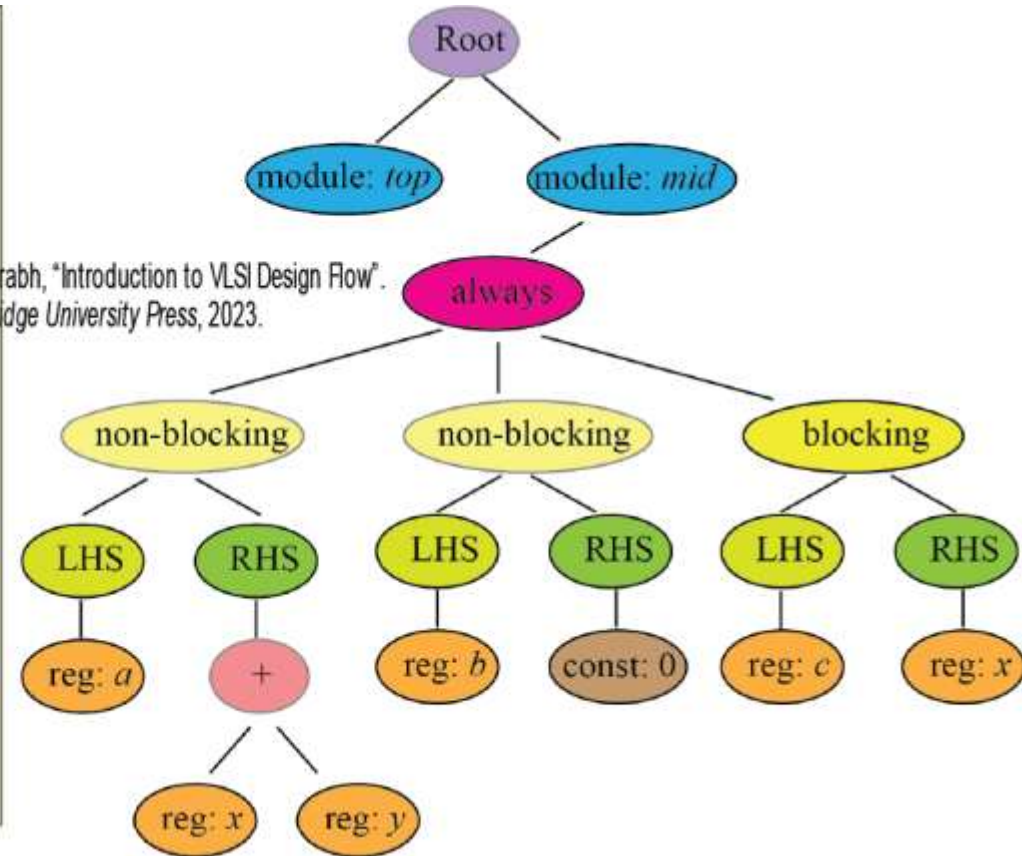S. Saurabh, "Introduction to VLSI Design Flow".
Cambridge University Press, 2023.



RTL Synthesis: Elaboration (1)

- Checks whether the connections among RTL-specified components are legitimate.
 - If legitimate, then make connections in the internal model; else report error

```
module leaf(d, clk, q);  
input d, clk;  
output q;  
...  
endmodule
```

```
module middle(D, CLK, Q);  
input D, CLK;  
output Q;  
  
leaf F1(d(D), .clk(CLK), .q(Q));  
  
endmodule
```


```
module Top(data, clk, result);  
input data, clk;  
output result;  
wire w1, w2;
```

```
leaf I1(d(data), .clk(clk),  
.q(w1));
```


```
leaf I2(d(w1), .clk(clk),  
.q(w2));
```

```
middle I3(D(w2),  
.Q(result), .CLK(clk));
```

```
endmodule
```

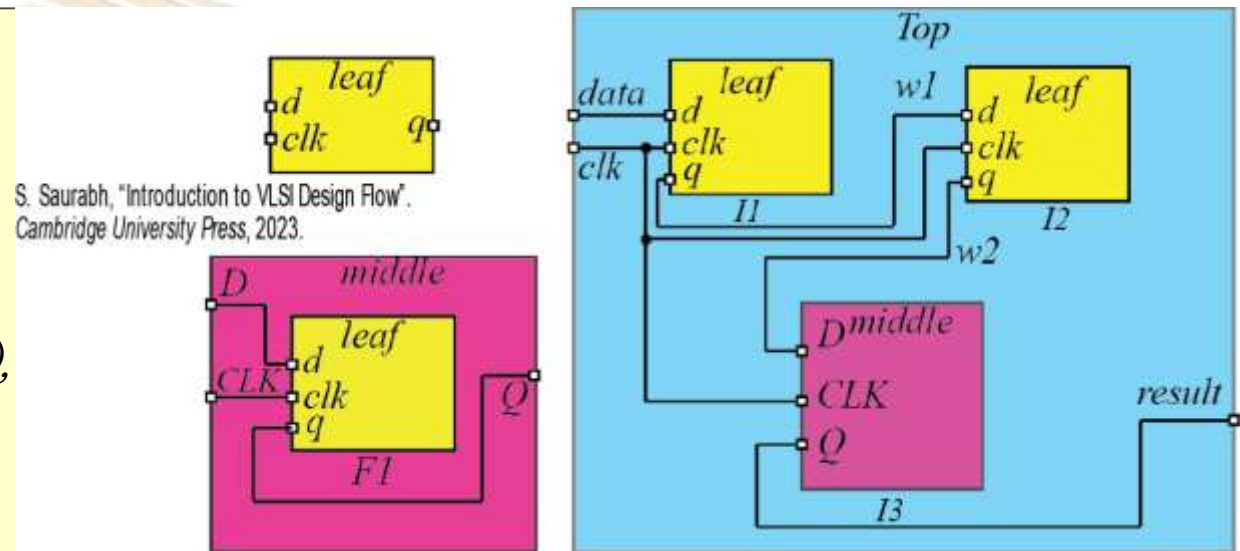


RTL Synthesis: Elaboration (2)

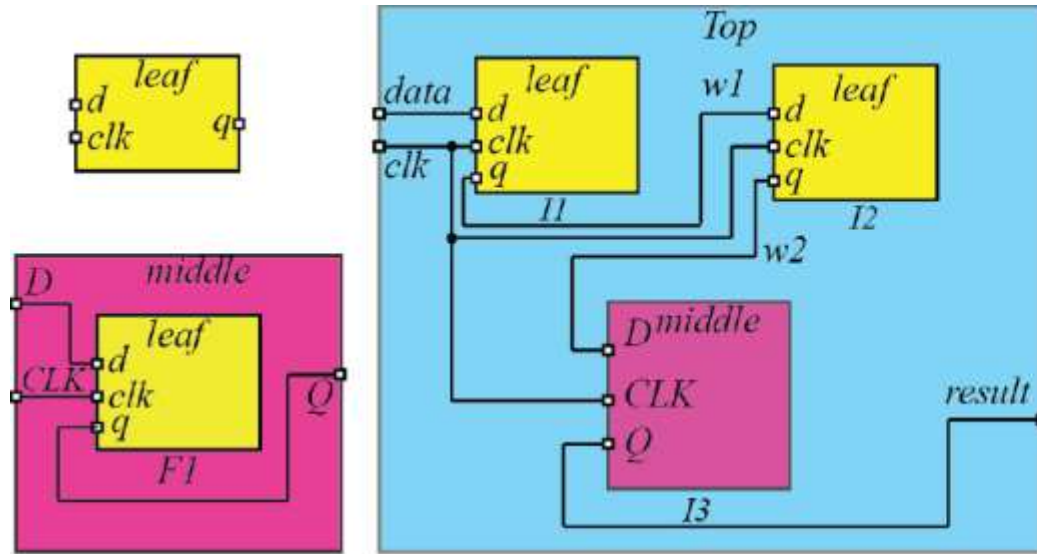

Before Elaboration

 S. Saurabh, "Introduction to VLSI Design Flow". Cambridge University Press, 2023.



After Elaboration


RTL Synthesis: Elaboration (3)

- Elaboration needs to process parameterized modules
 - Parameterized modules can have different interfaces for varying parameters.
- Creates separate modules with different interfaces for each distinct set of parameters

```
module counter(clk, rst,  
              count),  
    parameter WIDTH=4;  
    input clk, rst,  
    output [WIDTH-1:0]count,  
    reg [WIDTH-1:0]count,  
    ...  
endmodule
```

```
module top(clk, rst, count1, count2,  
          count3);  
    input clk, rst,  
    output [15:0]count1,  
    output [7:0]count2,  
    output [3:0]count3,  
  
    counter C1(clk, rst, count3);  
    counter #(8) C2(clk, rst, count2);  
    counter #(.WIDTH(16)) C3(clk, rst,  
                             count1);  
  
endmodule
```

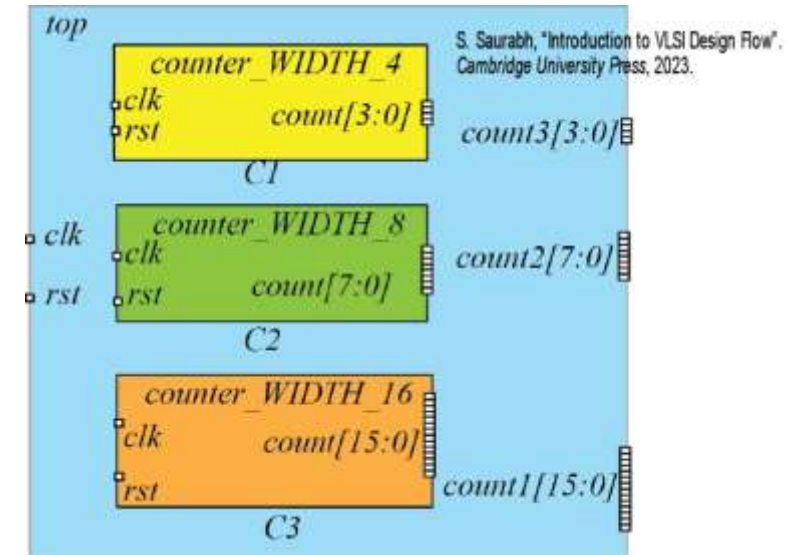S. Saurabh, "Introduction to VLSI Design Flow". Cambridge University Press, 2023.



RTL Synthesis



Verilog Constructs to
Circuit

Synthesizable and Non-synthesizable Constructs

- Some Verilog constructs cannot be synthesized into circuit elements
 - They are helpful in other design tasks such as functional verification

- A given RTL synthesis tool may not support all synthesizable Verilog constructs or modeling styles.
 - Need to be aware of the Verilog constructs supported by the synthesis tool used in design implementation

Typically non-synthesizable:


- Delay specification:
 - `out1 <= #12 a;` treated as `out1 <= a;`
- initial block
- fork, join, force, release
- data types real and time
- \$display, \$monitor, and other system tasks

NPTEL

Assign Statement

- Combinational circuit elements inferred

```
module top(a, b, c, p, q, s, x, y, out1, out2, out3);  
    input a, b, c, p, q, s;  
    input [3:0]x, y;  
    output out1;  
    output [3:0]out2;  
    output out3;  
  
    assign out1 = (a & b) | c; // logic network  
    assign out2 = (x & y); // bitwise logic network  
    assign out3 = (s) ? q : p; // multiplexer  
  
endmodule
```

 


S. Saurabh, "Introduction to VLSI Design Flow". Cambridge University Press, 2023.

If-else Statement

- Multiplexer or selecting logic inferred

```
module top(a, b, s, out1);  
  input a, b, s;  
  output out1;  
  reg out1;  
  
  always @(*) begin  
    if (s==1'b0)  
      out1 = a;  
    else  
      out1 = b;  
  end  
  
endmodule
```

 S. Saurabh, "Introduction to VLSI Design Flow". Cambridge University Press, 2023.




S. Saurabh, "Introduction to VLSI Design Flow". Cambridge University Press, 2023.

Case Statement

- Multiplexer or selecting logic inferred


```
module top(a, b, c, d, s, out1);
    input a, b, c, d;
    input [1:0]s;
    output out1;
    reg out1;

     always @(*) begin
        case (s)
            2'b00: out1 = a;
            2'b01: out1 = b;
            2'b10: out1 = c;
            2'b11: out1 = d;
            default: out1=a;
        endcase
    end
endmodule
```



```
module top(a, b, c, s, out1);
    input a, b, c;
    input [1:0]s;
    output out1;
    reg out1;

     always @(*) begin
        case (s)
            2'b1?: out1 = a;
            2'b?1: out1 = b;
            default: out1=c;
        endcase
    end
endmodule
```



If-else-if with priority will be synthesized similarly

Synthesis of Always Block


- Always block can be synthesized to combinational logic, latches, or flip-flop
- Depends on the sensitivity list and how are variables assigned with the always block



Always Block: Edge-sensitive


Flip-flops are inferred for edge-sensitive always blocks
 
```
module DFlipFlop(d, clk, q);  
    input d, clk;  
    output q;  
    reg q;  
  
    always @ ( posedge clk)  
        q <= d;  
  
endmodule
```




S. Saurabh, "Introduction to VLSI Design Flow".
Cambridge University Press, 2023.
 
```
module AsyncRstFlipFlop(d, clk, q, rst);  
    input d, clk, rst;  
    output q;  
    reg q;  
  
    always @ ( posedge clk or  
        negedge rst)  
        if (rst == 1'b0) begin  
            q <= 1'b0;  
        end else begin  
            q <= d;  
        end  
  
endmodule
```



S. Saurabh, "Introduction to VLSI Design Flow".
Cambridge University Press, 2023.
 
```
module SyncRstFlipFlop(d, clk,  
    q, rst);  
    input d, clk, rst;  
    output q;  
    reg q;  
  
    always @ ( posedge clk)  
        if (rst == 1'b0) begin  
            q <= 1'b0;  
        end else begin  
            q <= d;  
        end  
  
endmodule
```




S. Saurabh, "Introduction to VLSI Design Flow".
Cambridge University Press, 2023.


Always Block: Blocking and Non-blocking Assignments

Handling of blocking and non-blocking assignments in always block done differently (follows the semantics of simulation).
 
```
module top1(in1, clk, out1);  
  input in1, clk;  
  output out1;  
  reg reg1, reg2, reg3, out1;  
  
  always @ ( posedge clk)  
  begin  
    reg1 = in1;  
    reg2 = reg1;  
    reg3 = reg2;  
    out1 = reg3;  
  end  
endmodule
```


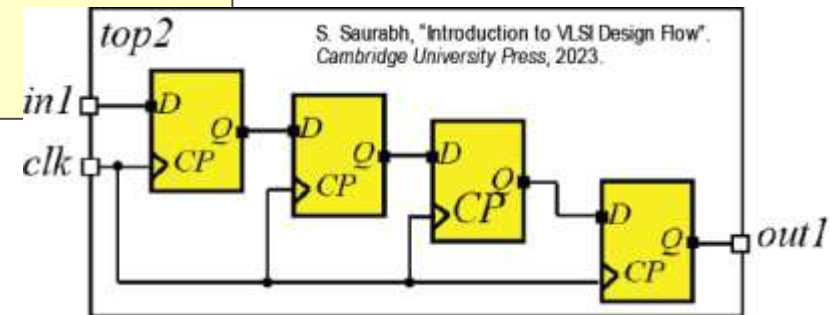
```
module top2(in1, clk, out1);  
  input in1, clk;  
  output out1;  
  reg reg1, reg2, reg3, out1;  
  
  always @ ( posedge clk)  
  begin  
    reg1 <= in1;  
    reg2 <= reg1;  
    reg3 <= reg2;  
    out1 <= reg3;  
  end  
endmodule
```




Always Block: Level-sensitive

When always block does NOT contain edges in the sensitivity list, combinational circuit elements or latches are inferred.


- **Combinational elements:** when the value of a variable is updated (refreshed) in every possible path (conditional branches in the code) within an always block
- **Latch:** if the variable retains its old value in some paths of the always block

```
module top(a, b, c, s, en, out1, out2);  
  input a, b, c, s, en;  
  output out1, out2;  
  reg out1, out2;  
  
  always @(*) begin  
    if (s==1'b0)  
      out1 = a;  
    else  
      out1 = b;  
  end  
  
  always @(*) begin  
    if (en==1'b1)  
      out2 = c;  
  end  
endmodule
```
 
```
always @(*) begin  
  if (en==1'b1) out2 = c;  
  else out2 = out2;  
end
```



 S. Saurabh, "Introduction to VLSI Design Flow",
Cambridge University Press, 2023.



S. Saurabh, "Introduction to VLSI Design Flow",
Cambridge University Press, 2023.

Always Block: Unintentional Latch Inference

- Latches often get inferred due to incorrect modeling of a combinational block
- Example: inadvertently miss updating value in one of the branches of a case statement.

To avoid such problems:

- Use default case to cover all possible paths in a case statement.
- Set the output of a combinational logic to a default value at the beginning of the always block

```
module top(in1, out1);  
    input [0:1]in1;  
    output out1;  
    reg out1;  
  
    always @* begin  
        case(in1[0:1])  
            2'b00: out1 = 1'b0;  
            2'b01: out1 = 1'b1;  
            2'b10: out1 = 1'b1;  
        endcase  
    end  
endmodule
```

S. Saurabh, "Introduction to VLSI Design Flow". Cambridge University Press, 2023.

References

- S. Saurabh, “Introduction to VLSI Design Flow”. Cambridge: *Cambridge University Press*, 2023.

