


# VLSI DESIGN FLOW: RTL TO GDS

Lecture 13  
RTL Synthesis- Part II



Sneh Saurabh  
Electronics and Communications  
Engineering  
IIT Delhi

# Lecture Plan

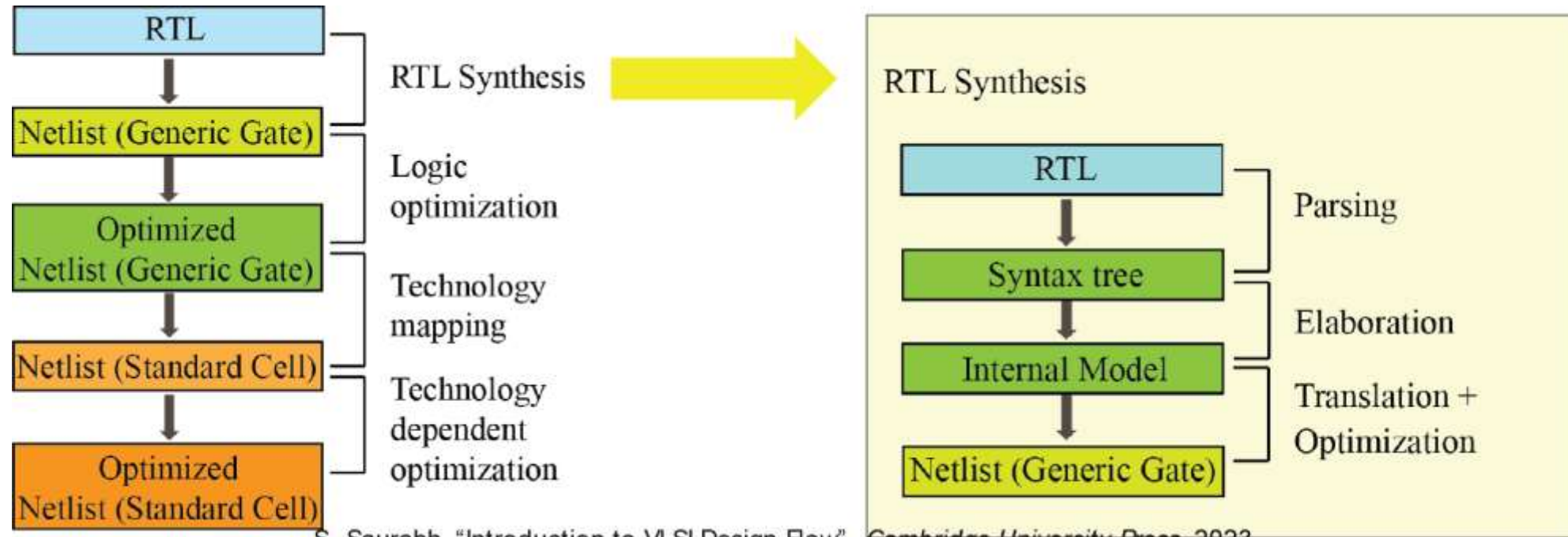

S. Saurabh, "Introduction to VLSI Design Flow". Cambridge University Press, 2023.

- Translation of some more Verilog Constructs to Circuit
- Optimization

---

---

The NPTEL logo is a circular emblem with a stylized flower or sunburst in the center, surrounded by a ring of colored segments. The word "NPTEL" is written in large, bold, orange letters below the emblem.

# RTL Synthesis




Verilog Constructs to  
Circuit

# For Loop

- A for loop can model repeated logic structure
- RTL synthesis tool can unroll (expand) the loop and instantiate circuit elements for each iteration.
  - Must know the number of iterations during synthesis (not during runtime)
  - Synthesizable for a fixed number of iterations

```
module top(a, b, cin, sum, cout);  
  input [3:0]a, b; input cin;  
  output [3:0]sum; output cout;  
  reg [3:0]sum; reg cout; reg carry;  
  reg [2:0]idx;  
  
  always @(*) begin  
    carry = cin;  
    for(idx=0; idx < 4; idx=idx+1)  
      begin  
        {carry, sum[idx]} =  
          a[idx] + b[idx] + carry;  
      end  
    cout = carry;  
  end  
  
endmodule
```
 
```
{carry, sum[0]}=a[0]+b[0]+cin;  
{carry, sum[1]}=a[1]+b[1]+carry;  
{carry, sum[2]}=a[2]+b[2]+carry;  
{cout, sum[3]}=a[3]+b[3]+carry;
```




S. Saurabh, "Introduction to VLSI Design Flow".  
Cambridge University Press, 2023.
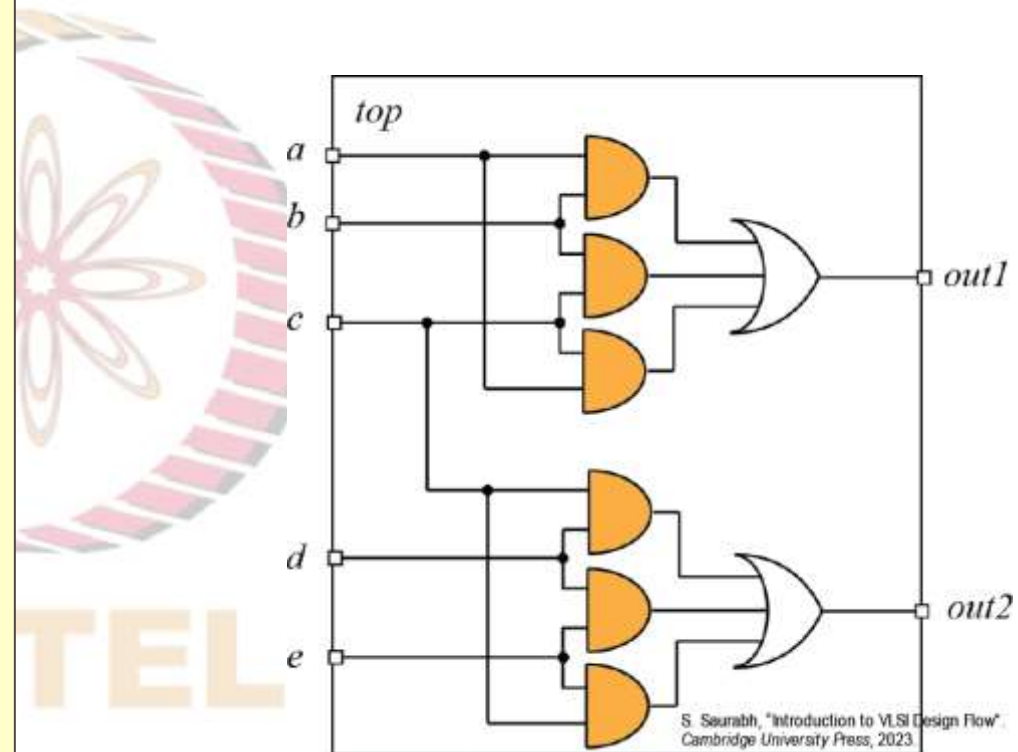
# Functions

Function synthesizes to a combinational logic block with one output (scalar or vector).

```
module top(a, b, c, d, e, out1, out2);  
  input a, b, c, d, e;  
  output out1, out2;  
  reg out2;  
  
  function MAJOR3;  
    input A, B, C;  
    begin  
      MAJOR3 = (A&B)/(B&C)/(C&A);  
    end  
  endfunction  
  
  assign out1 = MAJOR3(a, b, c);  
  
  always @(*) begin  
    out2 = MAJOR3(c, d, e);  
  end  
  
endmodule
```



# Operators: Synthesis Tasks

---

## Operators:

- Verilog supports various kinds of operators
  - Logical: operators `!`, `&&`, `||` etc.
  - Bitwise operators: `~`, `!`, `|`, `^`, `~^` etc.
  - Arithmetic operators: `+`, `-`, `*` / `/` etc.
  - Relational: `<`, `>`, `==` etc.

## Arithmetic and relational operators:

- Translate them to an internal representation or data structure
- Perform operator-level optimization
- Map operators to specific implementation

- Directly translate logical and bit-wise operators to their corresponding logic gates and optimize them subsequently.

---

---



RTL Synthesis





Resource/Timing  
Optimization
  
# Operators: Resource Sharing

```
if (sel == 1'b0)
    z = a*b;
else
    z = x*y;
```

Assume:  $a, b, x, y$  are of 8 bits and  $z$  is of 16 bits.



- Critical path can change
- Need to ensure that path through the select pin of the multiplexer does not violate timing constraint




# Operators: Speculation (Resource Unsharing)

```
if (sel == 1'b0)
    y = b;
else
    y = c;

z = a + y;
```

 Assume:  $a$ ,  $b$ ,  $c$ ,  $y$  are of 8 bits.



- Assume that path through  $sel$  is critical.

- Decreases delay of the critical path by employing more resources
- Performs addition irrespective of the sum being needed
  - speculation or eager computation

---

# RTL Synthesis



Implementation of  
Arithmetic Function

# Operators: Implementation

- Tools map arithmetic operators to predefined modules implementing these operators.
- A set of internal parameterized modules implementing arithmetic operators (+, −, \*, /) and relational operators (==, >, >=, <, <=).
- Instantiate these internal modules and choose the right set of parameters




# Operators: Implementation Example

```
module top(a, b, c, d, sum, carry, comp);  
  input [7:0]a, b, c, d;  
  output [7:0]sum;  
  output carry, comp;  
  
  assign {carry,sum}= a + b;  
  assign comp = (c > d);  
  
endmodule
```

S. Saurabh, "Introduction to VLSI Design Flow". Cambridge University Press, 2023.

 - Exact implementation tool-specific (logical function same)
- Architecture switching in later stages possible




---

---




RTL Synthesis

 

Compiler Optimizations
 
# Compiler Optimizations

- Adapt compiler optimization techniques to RTL synthesis
- Can be applied to the parse tree or the internal model of the RTL
  - Typically, optimizations applied in passes
- Gives significant gains for arithmetic operators



# Compiler Optimizations: Examples

**Constant Propagation:** replace expression with constant when possible

```
a = 8*8;  
b = (a*1024)/32;  
c = (b+32+b+32);
```

```
a = 64;  
b = 2048;  
c = 4160;
```

**Common subexpression elimination:** replace identical subexpression in multiple expressions with a single variable if it reduces the cost, such as area

```
x = p+a*b;  
y = q+a*b;
```

```
c = a*b;  
x = p+c;  
y = q+c;
```

**Strength reduction:** replace an expensive arithmetic operation with an equivalent less expensive operation

```
x = a*64;  
y = b/4;  
z = c*17;
```

```
x = a<<6;  
y = b>>2;  
z = (c<<4)+c;
```

S. Saurabh, "Introduction to VLSI Design Flow". *Cambridge University Press*, 2023.

# References

---

- G. D. Micheli. “Synthesis and Optimization of Digital Circuits”. *McGraw-Hill Higher Education*, 1994.
- S. Saurabh, “Introduction to VLSI Design Flow”. Cambridge: *Cambridge University Press*, 2023.

