
# VLSI DESIGN FLOW: RTL TO GDS

Lecture 28
Timing-driven Optimizations

 


Sneh Saurabh Electronics and Communications Engineering IIIT Delhi

### Lecture Plan



# Timing-driven Optimization: Flow

 

# Timing Driven Optimization: Resizing

- Libraries contain cells of same functionality and different sizes
  - Size of the cell increases, delay decreases

**Example:** cell *C1* replaced with a functionally equivalent cell *C2* of a larger size

#### **Effects:**

- 1. Delay and output slew of *C2* can reduce
  - ➤ Delay of cells in the fanout of *C2* can also reduce
- 2. Delay and output slew of the driver of *C2* can increase
  - ➤ Delay of the cells in its fanout, including that of C2, can increase


#### Resizing:

 Replace a cell C1 with another cell C2 that produces the same Boolean function but has a different size


### Timing Driven Optimization: Restructure (1)
 
#### Rewiring:

 Timing critical signals are moved closer to the sink in a cone of logic to reduce the overall path delay


 
### Timing Driven Optimization: Restructure (2)




$$Y = F(x_0, x_1, x_2, \dots, x_N)$$


- Let  $x_0$  be the signal that arrives last (AT of  $x_0$  is greatest) and is on the critical path
- How to restructure the circuit such that the worst delay of the circuit improves?
 
#### **Shannon Expansion**

- $F_0 = F(0, x_1, x_2, ..., x_N)$
- $F_1 = F(1, x_1, x_2, ..., x_N)$




### Restructure: Illustration

 

$$Z = F(A, B, C) = AB + C$$

$$F_{B=0} = C$$


$$F_{B=1} = A + C$$

 

Arrival Time: 130 ps

 
### Fanout Optimization

Fanout optimization: inserting buffers in a high-fanout


 
## Retiming

Retiming: balance the amount of logic between registers



### References

• S. Saurabh, "Introduction to VLSI Design Flow". Cambridge: *Cambridge University Press*, 2023.

